

Digital Design and Computer Organization Laboratory

3rd Semester, Academic Year 2024

Date: 24/10/2024

Name: Rithvik Rajesh Matta	SRN: PES2UG23CS485	Section: H
-------------------------------	-----------------------	------------

Week# ____10____ Program Number: ____10__

Aim of the Experiment:


CONSTRUCT A PROGRAM COUNTER, FOR EVERY CLOCK CYCLE.GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE

I. Verilog Code Screenshot

week 10 - program counter > pc.v

```
1  module fa (input wire i0, i1, cin, output wire sum, cout);
2      wire t0, t1, t2;
3      xor3 _i0 (i0, i1, cin, sum);
4      and2 _i1 (i0, i1, t0);
5      and2 _i2 (i1, cin, t1);
6      and2 _i3 (cin, i0, t2);
7      or3 _i4 (t0, t1, t2, cout);
8  endmodule
9
10 module addsub (input wire addsub, i0, i1, cin, output wire sumdiff, cout);
11 wire t;
12 fa _i0 (i0, t, cin, sumdiff, cout);
13 xor2 _i1 (i1, addsub, t);
14 endmodule
15
16 module pc_slice (input wire clk, reset, cin, load, inc, sub, offset,
17 output wire cout, pc);
18 wire in, inc_;
19 invert invert_0 (inc, inc_);
20 and2 and2_0 (offset, inc_, t);
21 addsub addsub_0 (sub, pc, t, cin, in, cout);
22 dfxl dfxl_0 (clk, reset, load, in, pc);
23 endmodule
24
25 module pc_slice0 (input wire clk, reset, cin, load, inc, sub, offset, output wire cout, pc);
26 wire in;
27 or2 or2_0 (offset, inc, t);
28 addsub addsub_0 (sub, pc, t, cin, in, cout);
29 dfxl dfxl_0 (clk, reset, load, in, pc);
30 endmodule
31
32 module pc (input wire clk, reset, inc, add, sub, input wire [15:0] offset, output wire [15:0] pc);
33 input wire load;
34 input wire [15:0] c;
35 or3 or3_0 (inc, add, sub, load);
36 pc_slice0 pc_slice_0 (clk, reset, sub, load, inc, sub, offset[0], c[0], pc[0]);
37 pc_slice pc_slice_1 (clk, reset, c[0], load, inc, sub, offset[1], c[1], pc[1]);
38 pc_slice pc_slice_2 (clk, reset, c[1], load, inc, sub, offset[2], c[2], pc[2]);
39 pc_slice pc_slice_3 (clk, reset, c[2], load, inc, sub, offset[3], c[3], pc[3]);
40 pc_slice pc_slice_4 (clk, reset, c[3], load, inc, sub, offset[4], c[4], pc[4]);
41 pc_slice pc_slice_5 (clk, reset, c[4], load, inc, sub, offset[5], c[5], pc[5]);
42 pc_slice pc_slice_6 (clk, reset, c[5], load, inc, sub, offset[6], c[6], pc[6]);
43 pc_slice pc_slice_7 (clk, reset, c[6], load, inc, sub, offset[7], c[7], pc[7]);
44 pc_slice pc_slice_8 (clk, reset, c[7], load, inc, sub, offset[8], c[8], pc[8]);
45 pc_slice pc_slice_9 (clk, reset, c[8], load, inc, sub, offset[9], c[9], pc[9]);
46 pc_slice pc_slice_10 (clk, reset, c[9], load, inc, sub, offset[10], c[10], pc[10]);
47 pc_slice pc_slice_11 (clk, reset, c[10], load, inc, sub, offset[11], c[11], pc[11]);
48 pc_slice pc_slice_12 (clk, reset, c[11], load, inc, sub, offset[12], c[12], pc[12]);
49 pc_slice pc_slice_13 (clk, reset, c[12], load, inc, sub, offset[13], c[13], pc[13]);
50 pc_slice pc_slice_14 (clk, reset, c[13], load, inc, sub, offset[14], c[14], pc[14]);
51 pc_slice pc_slice_15 (clk, reset, c[14], load, inc, sub, offset[15], c[15], pc[15]);
52 endmodule
```

```

week 10 - program counter >  pc_tb.v
1  `timescale 1 ns / 100 ps
2  `define TESTVECS 5
3
4  module tb;
5      reg clk, reset, inc, add, sub;
6      reg [15:0] offset;
7      wire [15:0] pc;
8      reg [18:0] test_vecs [0:(`TESTVECS-1)];
9      integer i;
10     initial begin $dumpfile("tb_pc.vcd"); $dumpvars(0,tb); end
11     initial begin reset = 1'b1; #12.5 reset = 1'b0; end
12     initial clk = 1'b0; always #5 clk =~ clk;
13
14     initial begin
15         test_vecs[0][18] = 1'b1; test_vecs[0][17] = 1'b0; test_vecs[0][16] = 1'b0;
16         test_vecs[0][15:0] = 15'hxx;
17         test_vecs[1][18] = 1'b0; test_vecs[1][17] = 1'b1; test_vecs[1][16] = 1'b0;
18         test_vecs[1][15:0] = 15'ha5;
19         test_vecs[2][18] = 1'b0; test_vecs[2][17] = 1'b0; test_vecs[2][16] = 1'b0;
20         test_vecs[2][15:0] = 15'hxx;
21         test_vecs[3][18] = 1'b1; test_vecs[3][17] = 1'b0; test_vecs[3][16] = 1'b0;
22         test_vecs[3][15:0] = 15'hxx;
23         test_vecs[4][18] = 1'b0; test_vecs[4][17] = 1'b0; test_vecs[4][16] = 1'b1;
24         test_vecs[4][15:0] = 15'h14;
25     end
26
27     initial {inc, add, sub, offset} = 0;
28     pc_pc_0 (clk, reset, inc, add, sub, offset, pc);
29     initial begin
30         #6 for(i=0;i<`TESTVECS;i=i+1)
31             begin #10 {inc, add, sub, offset}=test_vecs[i]; end
32         #100 $finish;
33     end
34
35     always@(reset or inc or add or sub )
36
37     $monitor("At time = %t, Reset= %b,inc=%b, add=%b,sub = %b,pc =%h ", $time,reset,inc,add,sub,pc);
38
39     endmodule

```

II. Verilog VVP Output Screen Shot

```




● rithvikmatta@penguin:~/PES/DDCO-sem-3/week 10 - program counter$ iverilog -o test lib.v pc.v pc_tb.v
● rithvikmatta@penguin:~/PES/DDCO-sem-3/week 10 - program counter$ vvp test
VCD info: dumpfile tb_pc.vcd opened for output.
At time =          0, Reset= 1,inc=0, add=0,sub = 0,pc =xxxx
At time =         50, Reset= 1,inc=0, add=0,sub = 0,pc =0000
At time =        130, Reset= 0,inc=0, add=0,sub = 0,pc =0000
At time =        160, Reset= 0,inc=1, add=0,sub = 0,pc =0000
At time =        250, Reset= 0,inc=1, add=0,sub = 0,pc =0001
At time =        260, Reset= 0,inc=0, add=1,sub = 0,pc =0001
At time =        350, Reset= 0,inc=0, add=1,sub = 0,pc =00a6
At time =        360, Reset= 0,inc=0, add=0,sub = 0,pc =00a6
At time =        460, Reset= 0,inc=1, add=0,sub = 0,pc =00a6
At time =        550, Reset= 0,inc=1, add=0,sub = 0,pc =00a7
At time =        560, Reset= 0,inc=0, add=0,sub = 1,pc =00a7
At time =        650, Reset= 0,inc=0, add=0,sub = 1,pc =0093
At time =        750, Reset= 0,inc=0, add=0,sub = 1,pc =007f
At time =        850, Reset= 0,inc=0, add=0,sub = 1,pc =006b
At time =        950, Reset= 0,inc=0, add=0,sub = 1,pc =0057
At time =       1050, Reset= 0,inc=0, add=0,sub = 1,pc =0043
At time =       1150, Reset= 0,inc=0, add=0,sub = 1,pc =002f
At time =       1250, Reset= 0,inc=0, add=0,sub = 1,pc =001b
At time =       1350, Reset= 0,inc=0, add=0,sub = 1,pc =0007
At time =       1450, Reset= 0,inc=0, add=0,sub = 1,pc =fff3
At time =       1550, Reset= 0,inc=0, add=0,sub = 1,pc =ffdf
● rithvikmatta@penguin:~/PES/DDCO-sem-3/week 10 - program counter$ gtkwave tb_pc.vcd


GTKWave Analyzer v3.3.118 (w)1999-2023 BSI

[0] start time.
[156000] end time.
GTKWAVE | Touch screen detected, enabling gestures.
Exiting.
● rithvikmatta@penguin:~/PES/DDCO-sem-3/week 10 - program counter$

```

III. GTKWAVE Screenshot

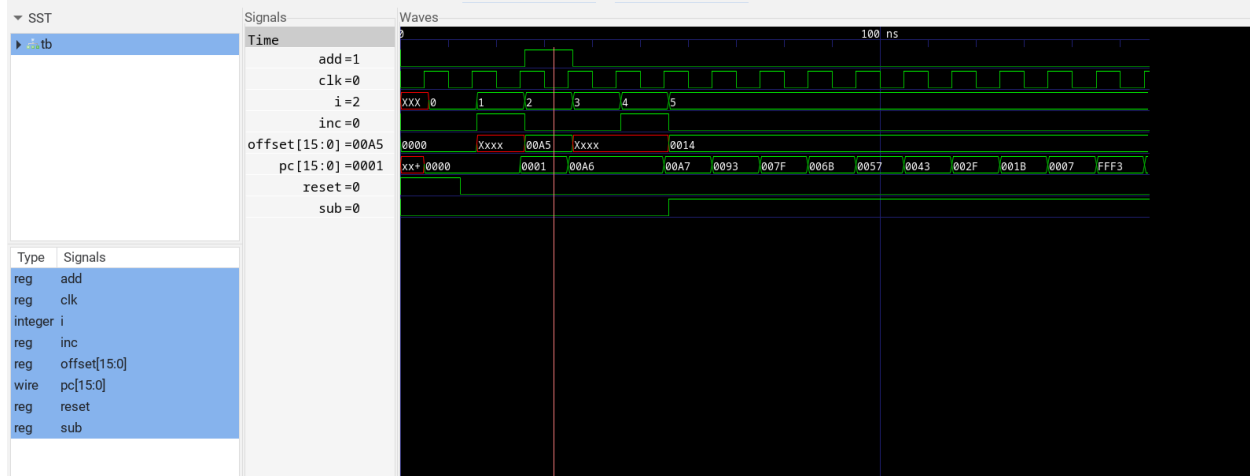 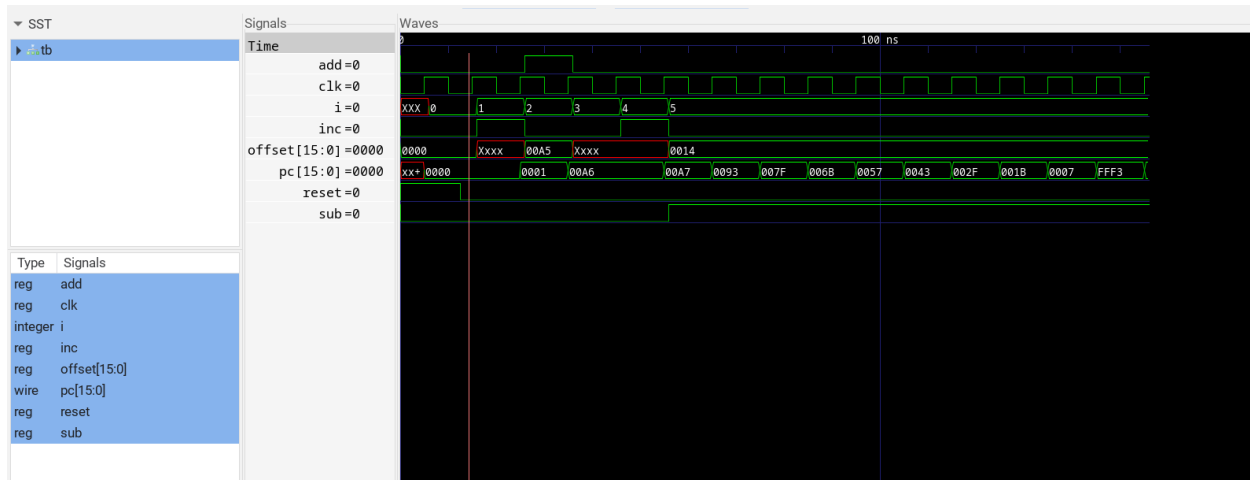

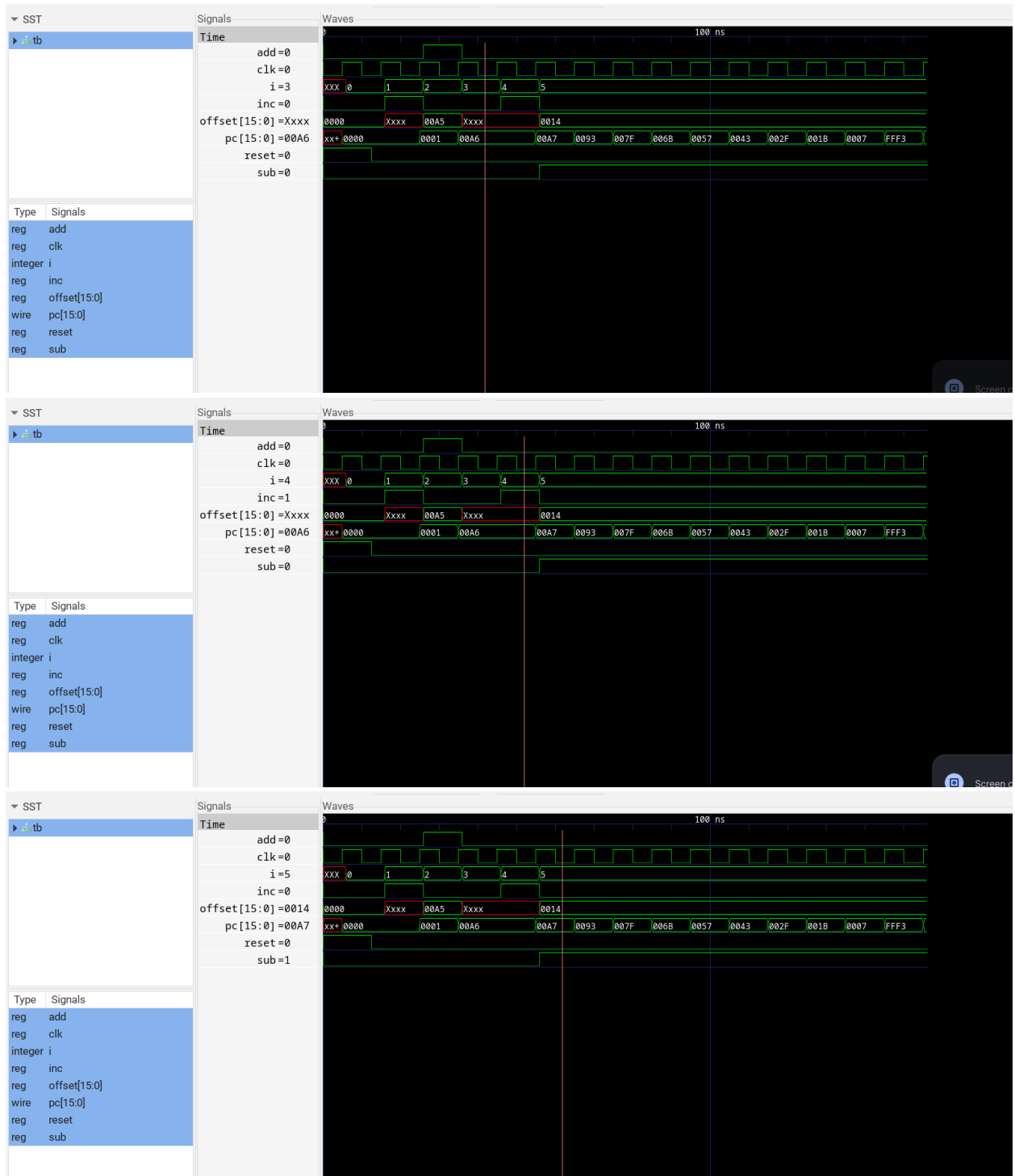

IV. Output Table (Truth Table)

Time	Reset	Inc	Add	Sub	PC
0	1	0	0	0	xxxx
50	1	0	0	0	0000

130	0	0	0	0	0000
160	0	1	0	0	0000
250	0	1	0	0	0001
260	0	0	1	0	0001
350	0	0	1	0	00a6
360	0	0	0	0	00a6
460	0	1	0	0	00a6
550	0	1	0	0	00a7
560	0	0	0	1	00a7
650	0	0	0	1	0093
750	0	0	0	1	007f
850	0	0	0	1	006b
950	0	0	0	1	0057
1050	0	0	0	1	0043
1150	0	0	0	1	002f
1250	0	0	0	1	001b
1350	0	0	0	1	0007
1450	0	0	0	1	fff3
1550	0	0	0	1	ffdf

If found plagiarized, I will abide with the disciplinary action of the University.

Signature:

Name: Rithvik Rajesh Matta

SRN: PES2UG23CS485

Section: H

Date: 24-10-2024