

Digital Design and Computer Organization Laboratory

3rd Semester, Academic Year 2024

Date: 3/10/2024

Name: Rithvik Rajesh Matta	SRN: PES2UG23CS485	Section: H
-------------------------------	-----------------------	------------

Week# ____ 6 ____

Program Number: ____ 6 ____

Aim of the Experiment:

CONSTRUCT A REGISTER FILE, FROM WHICH TWO 16-BIT VALUES CAN BE READ, AND TO WHICH ONE 16-BIT VALUE WRITTEN, EVERY CLOCK CYCLE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE

I. Verilog Code Screenshot

II. Verilog VVP Output Screen Shot

III. GTKWAVE Screenshot

IV. Output Table (Truth Table) to be completed
and included

- Code

week 6 > alu.v

```
1 module fa (input wire i0, i1, cin, output wire sum, cout);
2     wire t0, t1, t2;
3     xor3 _i0 (i0, i1, cin, sum);
4     and2 _i1 (i0, i1, t0);
5     and2 _i2 (i1, cin, t1);
6     and2 _i3 (cin, i0, t2);
7     or3 _i4 (t0, t1, t2, cout);
8 endmodule
9
10 module addsub (input wire addsub, i0, i1, cin, output wire sumdiff, cout);
11     wire t;
12     fa _i0 (i0, t, cin, sumdiff, cout);
13     xor2 _i1 (i1, addsub, t);
14 endmodule
15
16 module alu_slice ([input wire [1:0] op, input wire i0, i1, cin,
17 output wire o, cout]);
18     wire t_sumdiff, t_and, t_or, t_andor;
19     addsub _i0 (op[0], i0, i1, cin, t_sumdiff, cout);
20     and2 _i1 (i0, i1, t_and);
21     or2 _i2 (i0, i1, t_or);
22     mux2 _i3 (t_and, t_or, op[0], t_andor);
23     mux2 _i4 (t_sumdiff, t_andor, op[1], o);
24 endmodule
25
26 module alu (input wire [1:0] op, input wire [15:0] i0, i1,
27 output wire [15:0] o, output wire cout);
28     wire [14:0] c;
29     alu_slice _i0 (op, i0[0], i1[0], op[0], o[0], c[0]);
30     alu_slice _i1 (op, i0[1], i1[1], c[0], o[1], c[1]);
31     alu_slice _i2 (op, i0[2], i1[2], c[1], o[2], c[2]);
32     alu_slice _i3 (op, i0[3], i1[3], c[2], o[3], c[3]);
33     alu_slice _i4 (op, i0[4], i1[4], c[3], o[4], c[4]);
34     alu_slice _i5 (op, i0[5], i1[5], c[4], o[5], c[5]);
35     alu_slice _i6 (op, i0[6], i1[6], c[5], o[6], c[6]);
36     alu_slice _i7 (op, i0[7], i1[7], c[6], o[7], c[7]);
37     alu_slice _i8 (op, i0[8], i1[8], c[7], o[8], c[8]);
38     alu_slice _i9 (op, i0[9], i1[9], c[8], o[9], c[9]);
39     alu_slice _i10 (op, i0[10], i1[10], c[9], o[10], c[10]);
40     alu_slice _i11 (op, i0[11], i1[11], c[10], o[11], c[11]);
41     alu_slice _i12 (op, i0[12], i1[12], c[11], o[12], c[12]);
42     alu_slice _i13 (op, i0[13], i1[13], c[12], o[13], c[13]);
43     alu_slice _i14 (op, i0[14], i1[14], c[13], o[14], c[14]);
44     alu_slice _i15 (op, i0[15], i1[15], c[14], o[15], cout);
45 endmodule
```

```

F reg_alu.v M X
week 6 > F reg_alu.v
1 module reg16(input wire clk,reset,load,input wire [15:0]din,output wire [15:0]r);
2   df1 d0(clk,reset,load,din[0],r[0]);
3   df1 d1(clk,reset,load,din[1],r[1]);
4   df1 d2(clk,reset,load,din[2],r[2]);
5   df1 d3(clk,reset,load,din[3],r[3]);
6   df1 d4(clk,reset,load,din[4],r[4]);
7   df1 d5(clk,reset,load,din[5],r[5]);
8   df1 d6(clk,reset,load,din[6],r[6]);
9   df1 d7(clk,reset,load,din[7],r[7]);
10  df1 d8(clk,reset,load,din[8],r[8]);
11  df1 d9(clk,reset,load,din[9],r[9]);
12  df1 d10(clk,reset,load,din[10],r[10]);
13  df1 d11(clk,reset,load,din[11],r[11]);
14  df1 d12(clk,reset,load,din[12],r[12]);
15  df1 d13(clk,reset,load,din[13],r[13]);
16  df1 d14(clk,reset,load,din[14],r[14]);
17  df1 d15(clk,reset,load,din[15],r[15]);
18 endmodule
19
20 module reg_file (input wire clk, reset, wr, input wire [2:0] rd_addr_a,
21   rd_addr_b, wr_addr,
22   input wire [15:0] d_in, output wire [15:0] d_out_a, d_out_b);
23   wire [0:7]load;
24   wire [0:15]r0,r1,r2,r3,r4,r5,r6,r7;
25   demux8 dm8(wr,wr_addr[2],wr_addr[1],wr_addr[0],load);
26   reg16 reg0(clk,reset,load[0],d_in,r0);
27   reg16 reg1(clk,reset,load[1],d_in,r1);
28   reg16 reg2(clk,reset,load[2],d_in,r2);
29   reg16 reg3(clk,reset,load[3],d_in,r3);
30   reg16 reg4(clk,reset,load[4],d_in,r4);
31   reg16 reg5(clk,reset,load[5],d_in,r5);
32   reg16 reg6(clk,reset,load[6],d_in,r6);
33   reg16 reg7(clk,reset,load[7],d_in,r7);
34   mux128_16 mm0(r0,r1,r2,r3,r4,r5,r6,r7,rd_addr_a[0],rd_addr_a[1],
35     rd_addr_a[2],d_out_a);
36   mux128_16 mm1(r0,r1,r2,r3,r4,r5,r6,r7,rd_addr_b[0],rd_addr_b[1],
37     rd_addr_b[2],d_out_b);
38 endmodule
39
40 module mux128_16(input wire [15:0]i0,i1,i2,i3,i4,i5,i6,i7,input wire s0,s1,s2,
41   output wire [15:0]o);
42   mux8 mx0((i0[0],i1[0],i2[0],i3[0],i4[0],i5[0],i6[0],i7[0]),s2,s1,s0,o[0]);
43   mux8 mx1((i0[1],i1[1],i2[1],i3[1],i4[1],i5[1],i6[1],i7[1]),s2,s1,s0,o[1]);
44   mux8 mx2((i0[2],i1[2],i2[2],i3[2],i4[2],i5[2],i6[2],i7[2]),s2,s1,s0,o[2]);
45   mux8 mx3((i0[3],i1[3],i2[3],i3[3],i4[3],i5[3],i6[3],i7[3]),s2,s1,s0,o[3]);
46   mux8 mx4((i0[4],i1[4],i2[4],i3[4],i4[4],i5[4],i6[4],i7[4]),s2,s1,s0,o[4]);
47   mux8 mx5((i0[5],i1[5],i2[5],i3[5],i4[5],i5[5],i6[5],i7[5]),s2,s1,s0,o[5]);
48   mux8 mx6((i0[6],i1[6],i2[6],i3[6],i4[6],i5[6],i6[6],i7[6]),s2,s1,s0,o[6]);
49   mux8 mx7((i0[7],i1[7],i2[7],i3[7],i4[7],i5[7],i6[7],i7[7]),s2,s1,s0,o[7]);
50   mux8 mx8((i0[8],i1[8],i2[8],i3[8],i4[8],i5[8],i6[8],i7[8]),s2,s1,s0,o[8]);
51   mux8 mx9((i0[9],i1[9],i2[9],i3[9],i4[9],i5[9],i6[9],i7[9]),s2,s1,s0,o[9]);
52   mux8 mx10((i0[10],i1[10],i2[10],i3[10],i4[10],i5[10],i6[10],i7[10]),s2,s1,s0,o[10]);
53   mux8 mx11((i0[11],i1[11],i2[11],i3[11],i4[11],i5[11],i6[11],i7[11]),s2,s1,s0,o[11]);
54   mux8 mx12((i0[12],i1[12],i2[12],i3[12],i4[12],i5[12],i6[12],i7[12]),s2,s1,s0,o[12]);
55   mux8 mx13((i0[13],i1[13],i2[13],i3[13],i4[13],i5[13],i6[13],i7[13]),s2,s1,s0,o[13]);
56   mux8 mx14((i0[14],i1[14],i2[14],i3[14],i4[14],i5[14],i6[14],i7[14]),s2,s1,s0,o[14]);
57   mux8 mx15((i0[15],i1[15],i2[15],i3[15],i4[15],i5[15],i6[15],i7[15]),s2,s1,s0,o[15]);
58 endmodule
59
60 module mux2for16(input wire [15:0] din_regular, alu_out, input wire selector,
61   output wire [15:0]din_final);
62   mux2 m0(din_regular[0], alu_out[0], selector, din_final[0]);
63   mux2 m1(din_regular[1], alu_out[1], selector, din_final[1]);
64   mux2 m2(din_regular[2], alu_out[2], selector, din_final[2]);
65   mux2 m3(din_regular[3], alu_out[3], selector, din_final[3]);
66   mux2 m4(din_regular[4], alu_out[4], selector, din_final[4]);
67   mux2 m5(din_regular[5], alu_out[5], selector, din_final[5]);
68   mux2 m6(din_regular[6], alu_out[6], selector, din_final[6]);
69   mux2 m7(din_regular[7], alu_out[7], selector, din_final[7]);
70   mux2 m8(din_regular[8], alu_out[8], selector, din_final[8]);
71   mux2 m9(din_regular[9], alu_out[9], selector, din_final[9]);
72   mux2 m10(din_regular[10], alu_out[10], selector, din_final[10]);
73   mux2 m11(din_regular[11], alu_out[11], selector, din_final[11]);
74   mux2 m12(din_regular[12], alu_out[12], selector, din_final[12]);
75   mux2 m13(din_regular[13], alu_out[13], selector, din_final[13]);

```

```

39
40 module mux128_16(input wire [15:0]i0,i1,i2,i3,i4,i5,i6,i7,input wire s0,s1,s2,
41 output wire [15:0]o);
42     mux8 mx0({i0[0],i1[0],i2[0],i3[0],i4[0],i5[0],i6[0],i7[0]},s2,s1,s0,o[0]);
43     mux8 mx1({i0[1],i1[1],i2[1],i3[1],i4[1],i5[1],i6[1],i7[1]},s2,s1,s0,o[1]);
44     mux8 mx2({i0[2],i1[2],i2[2],i3[2],i4[2],i5[2],i6[2],i7[2]},s2,s1,s0,o[2]);
45     mux8 mx3({i0[3],i1[3],i2[3],i3[3],i4[3],i5[3],i6[3],i7[3]},s2,s1,s0,o[3]);
46     mux8 mx4({i0[4],i1[4],i2[4],i3[4],i4[4],i5[4],i6[4],i7[4]},s2,s1,s0,o[4]);
47     mux8 mx5({i0[5],i1[5],i2[5],i3[5],i4[5],i5[5],i6[5],i7[5]},s2,s1,s0,o[5]);
48     mux8 mx6({i0[6],i1[6],i2[6],i3[6],i4[6],i5[6],i6[6],i7[6]},s2,s1,s0,o[6]);
49     mux8 mx7({i0[7],i1[7],i2[7],i3[7],i4[7],i5[7],i6[7],i7[7]},s2,s1,s0,o[7]);
50     mux8 mx8({i0[8],i1[8],i2[8],i3[8],i4[8],i5[8],i6[8],i7[8]},s2,s1,s0,o[8]);
51     mux8 mx9({i0[9],i1[9],i2[9],i3[9],i4[9],i5[9],i6[9],i7[9]},s2,s1,s0,o[9]);
52     mux8 mx10({i0[10],i1[10],i2[10],i3[10],i4[10],i5[10],i6[10],i7[10]},s2,s1,
53     s0,o[10]);
54     mux8 mx11({i0[11],i1[11],i2[11],i3[11],i4[11],i5[11],i6[11],i7[11]},s2,s1,
55     s0,o[11]);
56     mux8 mx12({i0[12],i1[12],i2[12],i3[12],i4[12],i5[12],i6[12],i7[12]},s2,s1,
57     s0,o[12]);
58     mux8 mx13({i0[13],i1[13],i2[13],i3[13],i4[13],i5[13],i6[13],i7[13]},s2,s1,
59     s0,o[13]);
60     mux8 mx14({i0[14],i1[14],i2[14],i3[14],i4[14],i5[14],i6[14],i7[14]},s2,s1,
61     s0,o[14]);
62     mux8 mx15({i0[15],i1[15],i2[15],i3[15],i4[15],i5[15],i6[15],i7[15]},s2,s1,
63     s0,o[15]);
64 endmodule
65
66 module mux2for16(input wire [15:0] din_regular, alu_out, input wire selector,
67 output wire [15:0]din_final);
68     mux2 m0(din_regular[0], alu_out[0], selector, din_final[0]);
69     mux2 m1(din_regular[1], alu_out[1], selector, din_final[1]);
70     mux2 m2(din_regular[2], alu_out[2], selector, din_final[2]);
71     mux2 m3(din_regular[3], alu_out[3], selector, din_final[3]);
72     mux2 m4(din_regular[4], alu_out[4], selector, din_final[4]);
73     mux2 m5(din_regular[5], alu_out[5], selector, din_final[5]);
74     mux2 m6(din_regular[6], alu_out[6], selector, din_final[6]);
75     mux2 m7(din_regular[7], alu_out[7], selector, din_final[7]);
76     mux2 m8(din_regular[8], alu_out[8], selector, din_final[8]);
77     mux2 m9(din_regular[9], alu_out[9], selector, din_final[9]);
78     mux2 m10(din_regular[10], alu_out[10], selector, din_final[10]);
79     mux2 m11(din_regular[11], alu_out[11], selector, din_final[11]);
80     mux2 m12(din_regular[12], alu_out[12], selector, din_final[12]);
81     mux2 m13(din_regular[13], alu_out[13], selector, din_final[13]);
82     mux2 m14(din_regular[14], alu_out[14], selector, din_final[14]);
83     mux2 m15(din_regular[15], alu_out[15], selector, din_final[15]);
84 endmodule
85
86
87 module reg_alu (input wire clk, reset, sel, wr, input wire [1:0] op,
88 input wire [2:0] rd_addr_a,
89 rd_addr_b, wr_addr, input wire [15:0] d_in,
90 output wire [15:0] d_out_a, d_out_b, output wire cout);
91     wire [15:0] alu_out;
92     wire [15:0] newdin;
93     mux2for16 select(d_in, alu_out, sel, newdin);
94     reg_file new_reg(clk, reset, wr, rd_addr_a, rd_addr_b,
95     wr_addr, newdin, d_out_a, d_out_b);
96     alu_calc(op, d_out_a, d_out_b, alu_out, cout);
97
98 endmodule

```

```

week 6 > E tb_reg_alu.v
1 `timescale 1 ns / 100 ps
2 `define TESTVECS 8
3
4 module tb;
5     reg clk, reset, wr, sel;
6     reg [1:0] op;
7     reg [2:0] rd_addr_a, rd_addr_b, wr_addr; reg [15:0] d_in;
8     wire [15:0] d_out_a, d_out_b;
9     reg [28:0] test_vecs [0:('TESTVECS-1)];
10    integer i;
11    initial begin $dumpfile("tb_reg_alu.vcd"); $dumpvars(0,tb); end
12    initial begin reset = 1'b1; #12.5 reset = 1'b0; end
13    initial clk = 1'b0; always #5 clk =~ clk;
14    initial begin
15        test_vecs[0][28] = 1'b0; test_vecs[0][27] = 1'b1; test_vecs[0][26:25] = 2'bxx;
16        test_vecs[0][24:22] = 3'ox; test_vecs[0][21:19] = 3'ox;
17        test_vecs[0][18:16] = 3'h3; test_vecs[0][15:0] = 16'hcdef;
18
19        test_vecs[1][28] = 1'b0; test_vecs[1][27] = 1'b1; test_vecs[1][26:25] = 2'bxx;
20        test_vecs[1][24:22] = 3'ox; test_vecs[1][21:19] = 3'ox;
21        test_vecs[1][18:16] = 3'o7; test_vecs[1][15:0] = 16'h3210;
22
23        test_vecs[2][28] = 1'b0; test_vecs[2][27] = 1'b1; test_vecs[2][26:25] = 2'bxx;
24        test_vecs[2][24:22] = 3'o3; test_vecs[2][21:19] = 3'o7;
25        test_vecs[2][18:16] = 3'o5; test_vecs[2][15:0] = 16'h4567;
26
27        test_vecs[3][28] = 1'b0; test_vecs[3][27] = 1'b1; test_vecs[3][26:25] = 2'bxx;
28        test_vecs[3][24:22] = 3'o1; test_vecs[3][21:19] = 3'o5;
29        test_vecs[3][18:16] = 3'o1; test_vecs[3][15:0] = 16'hba98;
30
31        test_vecs[4][28] = 1'b0; test_vecs[4][27] = 1'b0; test_vecs[4][26:25] = 2'bxx;
32        test_vecs[4][24:22] = 3'o1; test_vecs[4][21:19] = 3'o5;
33        test_vecs[4][18:16] = 3'o1; test_vecs[4][15:0] = 16'hxxxx;
34
35        test_vecs[5][28] = 1'b1; test_vecs[5][27] = 1'b1; test_vecs[5][26:25] = 2'b00;
36        test_vecs[5][24:22] = 3'o1; test_vecs[5][21:19] = 3'o5;
37        test_vecs[5][18:16] = 3'o2; test_vecs[5][15:0] = 16'hxxxx;
38
39        test_vecs[6][28] = 1'b1; test_vecs[6][27] = 1'b1; test_vecs[6][26:25] = 2'b01;
40        test_vecs[6][24:22] = 3'o2; test_vecs[6][21:19] = 3'o7;
41        test_vecs[6][18:16] = 3'o4; test_vecs[6][15:0] = 16'hxxxx;
42
43        test_vecs[7][28] = 1'b1; test_vecs[7][27] = 1'b0; test_vecs[7][26:25] = 2'b01;
44        test_vecs[7][24:22] = 3'o4; test_vecs[7][21:19] = 3'o4;
45        test_vecs[7][18:16] = 3'ox; test_vecs[7][15:0] = 16'hxxxx;
46    end
47    initial {sel, wr, op, rd_addr_a, rd_addr_b, wr_addr, d_in} = 0;
48    reg_alu reg_alu_0 (clk, reset, sel, wr, op, rd_addr_a, rd_addr_b, wr_addr, d_in,
49    d_out_a, d_out_b, cout);
50    initial begin
51        #6 for(i=0;i<'TESTVECS;i=i+1)
52            begin #10 {sel, wr, op, rd_addr_a, rd_addr_b, wr_addr, d_in}=test_vecs[i];
53        end
54        #100 $finish;
55    end
56
57    initial begin
58        $monitor($time = %t, Sel = %b, Wr = %b, Op = %b, RdAddrA = %b, RdAddrB = %b,
59        WrAddr = %b, DIn = %h, DOutA = %h, DOutB = %h, Cout = %b",
60        $time, sel, wr, op, rd_addr_a, rd_addr_b, wr_addr, d_in, d_out_a, d_out_b,
61        cout);
62    end
63
64 endmodule

```

• Terminal Output

```

rithvikmatta@penguin:~/PES/DDCO-sem-3/week 6$ iverilog -o test lib.v alu.v reg_alu.v tb_reg_alu.v
rithvikmatta@penguin:~/PES/DDCO-sem-3/week 6$ vvp test
VCD info: dumpfile tb_reg_alu.vcd opened for output.
Time = 0 , Sel = 0 , Wr = 0 , Op = 00 , RdAddrA = 000 , RdAddrB = 000 , WrAddr = 000 , DIn = 0000 , DOutA = xxxx , DOutB = xxxx , Cout = x
Time = 50 , Sel = 0 , Wr = 0 , Op = 00 , RdAddrA = 000 , RdAddrB = 000 , WrAddr = 000 , DIn = 0000 , DOutA = 0000 , DOutB = 0000 , Cout = 0
Time = 160 , Sel = 0 , Wr = 1 , Op = xx , RdAddrA = xxx , RdAddrB = xxx , WrAddr = 011 , DIn = cdef , DOutA = 0000 , DOutB = 0000 , Cout = x
Time = 250 , Sel = 0 , Wr = 1 , Op = xx , RdAddrA = xxx , RdAddrB = xxx , WrAddr = 011 , DIn = cdef , DOutA = XXXx , DOutB = XXXx , Cout = x
Time = 260 , Sel = 0 , Wr = 1 , Op = xx , RdAddrA = xxx , RdAddrB = xxx , WrAddr = 111 , DIn = 3210 , DOutA = XXXx , DOutB = XXXx , Cout = x
Time = 350 , Sel = 0 , Wr = 1 , Op = xx , RdAddrA = xxx , RdAddrB = xxx , WrAddr = 111 , DIn = 3210 , DOutA = xxxx , DOutB = xxxx , Cout = x
Time = 360 , Sel = 0 , Wr = 1 , Op = xx , RdAddrA = 011 , RdAddrB = 111 , WrAddr = 101 , DIn = 4567 , DOutA = 0000 , DOutB = 3210 , Cout = x
Time = 460 , Sel = 0 , Wr = 1 , Op = xx , RdAddrA = 001 , RdAddrB = 101 , WrAddr = 001 , DIn = ba98 , DOutA = 0000 , DOutB = 4567 , Cout = x
Time = 560 , Sel = 0 , Wr = 0 , Op = xx , RdAddrA = 001 , RdAddrB = 101 , WrAddr = 001 , DIn = xxxx , DOutA = 0000 , DOutB = 4567 , Cout = x
Time = 660 , Sel = 1 , Wr = 1 , Op = 00 , RdAddrA = 001 , RdAddrB = 101 , WrAddr = 010 , DIn = xxxx , DOutA = 0000 , DOutB = 4567 , Cout = 0
Time = 760 , Sel = 1 , Wr = 1 , Op = 01 , RdAddrA = 010 , RdAddrB = 111 , WrAddr = 100 , DIn = xxxx , DOutA = 4567 , DOutB = 3210 , Cout = 1
Time = 860 , Sel = 1 , Wr = 0 , Op = 01 , RdAddrA = 100 , RdAddrB = 100 , WrAddr = xxx , DIn = xxxx , DOutA = ba98 , DOutB = ba98 , Cout = 1
rithvikmatta@penguin:~/PES/DDCO-sem-3/week 6$ gtkwave tb_reg_alu.vcd

```

GTKWave Analyzer v3.3.118 (w)1999-2023 BSI

[0] start time.

[186000] end time.

GTKWAVE | Touch screen detected, enabling gestures.

Exiting.

- Gtkwave



0	1	xx	x	x	x	x	x	x	0	1	1	CDE F	Reg3= 0000
0	1	xx	x	x	x	x	x	x	1	1	1	3210	Reg7= 4567
0	1	xx	0	1	1	1	1	1	1	0	1	4567	Reg5= ba98
0	1	xx	0	0	1	1	0	1	0	0	1	BA9 8	Reg1= ba98
0	0	xx	0	0	1	1	0	1	0	0	1	xxxx	d_out_a=0000 d_out_b=4567
1	1	00	0	0	1	1	0	1	0	1	0	xxxx	Reg2=4567+BA98 =FFFF, cout =0
1	1	01	0	1	0	1	1	1	1	0	0	xxxx	Reg4 = FFFF-3210=CDEF, cout=1
1	0	01	1	0	0	1	0	0	x	x	x	xxxx	d_out_a- d_out_b= =CDEF- CDEF=0000